

Chapter 1 Assignment

1.5

List the relative advantages of digital systems compared to analog systems and vice versa.

1.13

How is an inverting amplifier different from a noninverting amplifier?

1.17

An FM radio receiver has an input resistance of 75Ω . The input signal provided by a distant transmitter is $5\mu V$ rms, and the receiver supplies $5V$ rms to an $8\text{-}\Omega$ loudspeaker. Calculate the power gain of the receiver.

1.27

A certain amplifier has an input voltage of $100mV$ rms and an input resistance of $100k\Omega$. It produces an output of $10V$ rms across an $8\text{-}\Omega$ load resistance.

The power supply has a voltage of $15V$ and delivers an average current of $2A$. Find the power dissipated in the amplifier and the efficiency of the amplifier.

1.51 Briefly discuss what the spectrum of a signal is and why it is important.

1.59 What is a differential amplifier?