

Diode Properties and the Circuits



Name _____ ID _____

Partners _____

Please be careful about touching the diode because the current heats up the part.

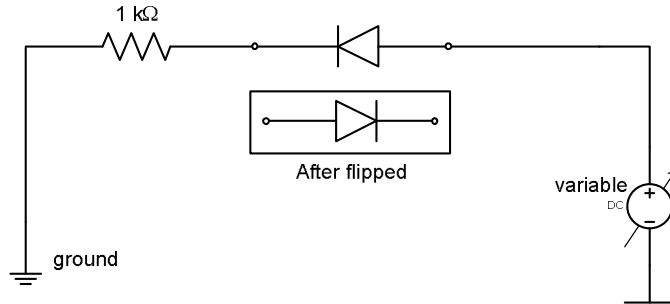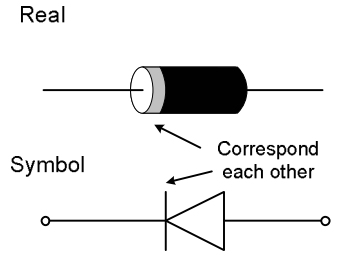1. A diode's property in DC voltage:

- Pick up the diode and make sure the direction. ⇒
- Make sure the provided circuit is appropriately arranged on the breadboard; you will measure the 5 currents with respect to the different voltages.




- Voltage is measured with a parallel circuit, and current is measured in a series circuit connection with multimeter.
You have to measure the voltages in the diode, NOT the resistor.
- Change the 5 voltages by following the data sheet.
- After the above measurement, flip the direction of the diode; then, measure the reversed currents for three different voltages. (Be careful! The diode might be very hot.)

Use the variable voltage source. (*Measure the voltage in the diode.*)

Forward bias		Reverse bias	
Voltage (V)	Current (mA)	Voltage (V)	Current (mA)
$V_c = 1\text{ V}$		$V_c = 1\text{ V}$	
$V_c = 2\text{ V}$		$V_c = 3\text{ V}$	
$V_c = 3\text{ V}$		$V_c = 5\text{ V}$	
$V_c = 4\text{ V}$		For reversed bias, the expression of voltage values is negative.	
$V_c = 5\text{ V}$			

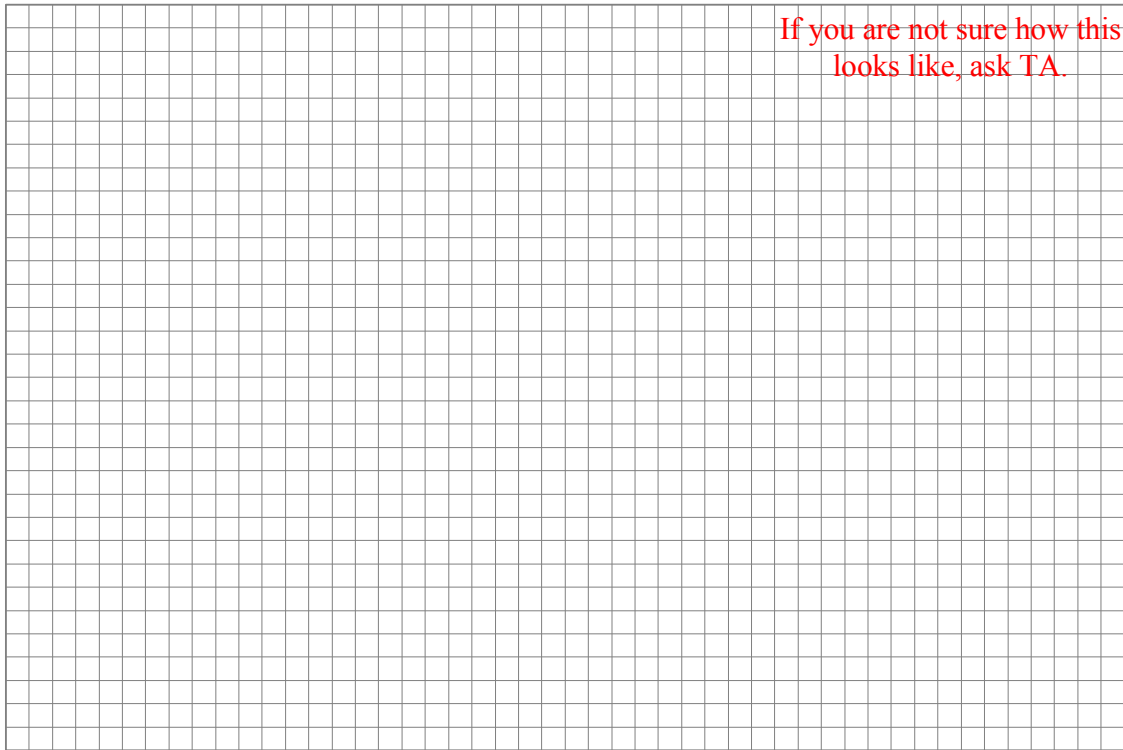
- **Plot the data on a graph sheet.**
The instructor will show the appropriate shape of the graph. Make sure if your graph is proper.




Question: Does the current increase exponentially (NOT linearly) for the forward bias?

2. A diode's property in AC voltage (Half-wave rectification):

- **Change the voltage sources from DC to AC.**
- **Connect the wires from the oscilloscope to the resistor, and display the voltage curves.**
 1. Voltage of R without diode; 2. Voltage of R with diode; 3. Voltage of R with flipped diode.

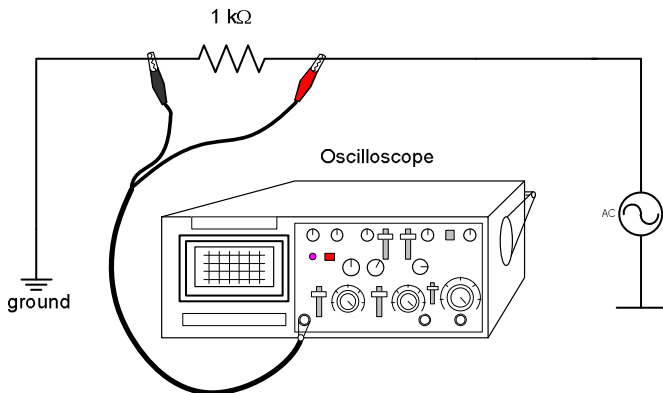


Case 1

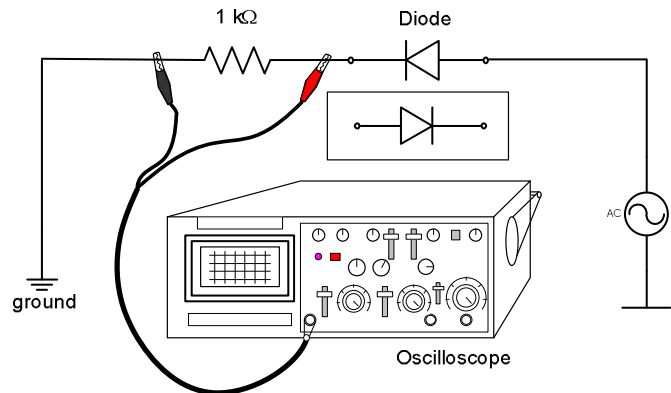

Cases 2 & 3

- Draw the voltage curves displayed on the oscilloscope under the following conditions.

 
- Case 1 Voltage in the resistor without the diode



- Case 2 Voltage in the resistor with the diode




 - Case 3 Voltage for the resistor after flipping the diode



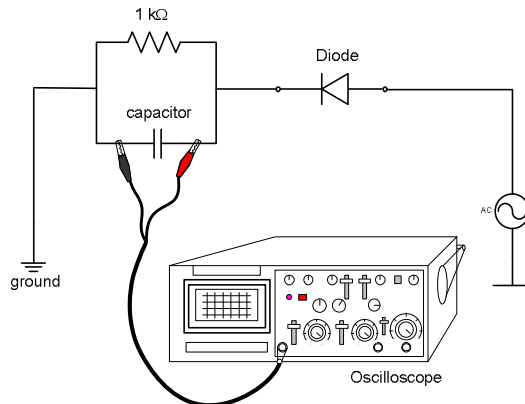3. RC circuit with diode

- Make the circuit and measure the voltage on the capacitor with the oscilloscope. Just sketch the voltage curve displayed on the oscilloscope.



- Voltage for the capacitor



4. A human antenna

- **Grab the oscilloscopes (+) and (ground) terminals with each hand; then touch the tip of the terminal with a finger.**
- **Adjust the scale of the frequency on the oscilloscope so that you can have the envelope waves.**
- **Read the period for the “envelope wave” and calculate the frequency.**
Frequency = 1 / period

The period of the envelope waves _____ (s)

The frequency of the envelope waves _____ (Hz) \Leftrightarrow *close to 60 Hz*